Pictures that add.

A toy bitmap machine, built entirely from NAND operations.

N = NAND(A, B)

L = NAND(A, N) R = NAND(B, N)

SUM = NAND(L, R)

CARRY = NAND(N, N)

A	B	SUM	CARRY
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

In the workbench, every pixel is an independent one-bit half-adder.

This is our own Boolean simulator, not JBIG2 and not an exploit reproduction.